

---

# A 1.25Gbit/s Serializer for LHC Data and Trigger Optical Links

*Paulo Moreira*

*CERN-EP/MIC, Geneva  
Switzerland*

# Outline

---

- LHC high-speed optical links
- Serializer “primer”
- ASIC architecture:
  - High-speed serializer
  - Clock generator
  - Phase-locked loop
- Testing the IC
- Summary

# LHC High-Speed Optical Links

---

- Gbit/s data links:
  - Sub-detectors  $\Leftrightarrow$  control/counting room
  - In data readout systems
    - Asynchronous data transmission is possible
  - In the trigger systems data path
    - Data transmission must be synchronous with the 40.08MHz LHC master clock

# LHC High-Speed Optical Links

---

- Typical configuration:
  - Unidirectional
- Transmitters inside the detectors:
  - Transmitters subject to high levels of radiation during the experiments lifetime
  - Large numbers  $\Rightarrow$  constrained power consumption

# LHC High-Speed Optical Links

---

- LHC high-speed links requirements:
  - Hardness to total dose radiation effects
  - Operation tolerant to SEU
  - Constant latency transmission for trigger systems (40.08 MHz synchronous)
  - Low power dissipation
  - Low cost

# LHC High-Speed Optical Links

---

- Can commercial devices fulfil HEP requirements?
  - Bandwidth (Yes)
  - Constant latency transmission (Yes, ...)
  - Radiation tolerance (No)
  - Operation tolerant to SEU (No)
  - Low power (?)
  - Low cost (?)

# LHC High-Speed Optical Links

---

- Radiation hardness: is there an alternative?
  - Specially hardened processes
- OR
- Mainstream sub- $\mu\text{m}$  CMOS processes  
+ radiation tolerant layout techniques

# LHC High-Speed Optical Links

---


- Why sub- $\mu\text{m}$  CMOS?
  - Today's semiconductor industry standard
  - Bandwidth capabilities exceed HEP requirements
  - Low power consumption
  - Price advantage when compared with any specially hardened technology
  - If used with radiation tolerant techniques
    - Very high resistance to total dose effects
    - Virtually single event latchup immune


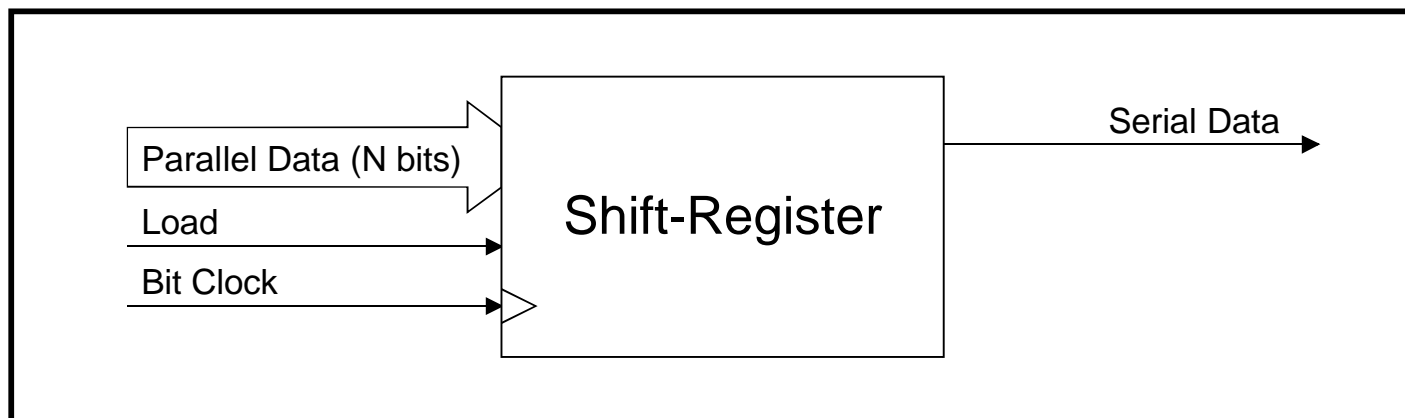
# Serializer “Primer”


---

- What is a serializer?
  - A shift register!
  - Parallel loaded at the “word rate”
  - “Emptied” at the “bit rate”
  - “Bit rate” = (#bits in word) × (data rate)


 
# Serializer “Primer”

- Parallel-load shift register:
  - cascade of flip-flops and 2-to-1 multiplexers
- Operation speed is limited by:
  - clock to Q delay
  - mux delay
  - flip-flop setup time
- Maximum frequency:
  - $1/(t_{cq} + t_{mux} + t_{setup})$




# Serializer “Primer”

---


- Operation @ 1.25GHz  $\Rightarrow T = 800\text{ps}$
- Static FF  $t(\text{min}) = 1292\text{ps}$  ! (worst case)
- Dynamic FF  $t(\text{min}) = 768\text{ps}$  (worst case)
- Can we use Dynamic FF?
  - **No, they are sensitive to SEU**

	DFF $t_{\text{pd}}$ (ps)	DFF $t_{\text{sup}}$ (ps)	SFF $t_{\text{pd}}$ (ps)	SFF $t_{\text{sup}}$ (ps)	MUX $t_{\text{pd}}$ (ps)
typical	145	60	309	107	104
worst	369	152	749	296	247


# ASIC Architecture

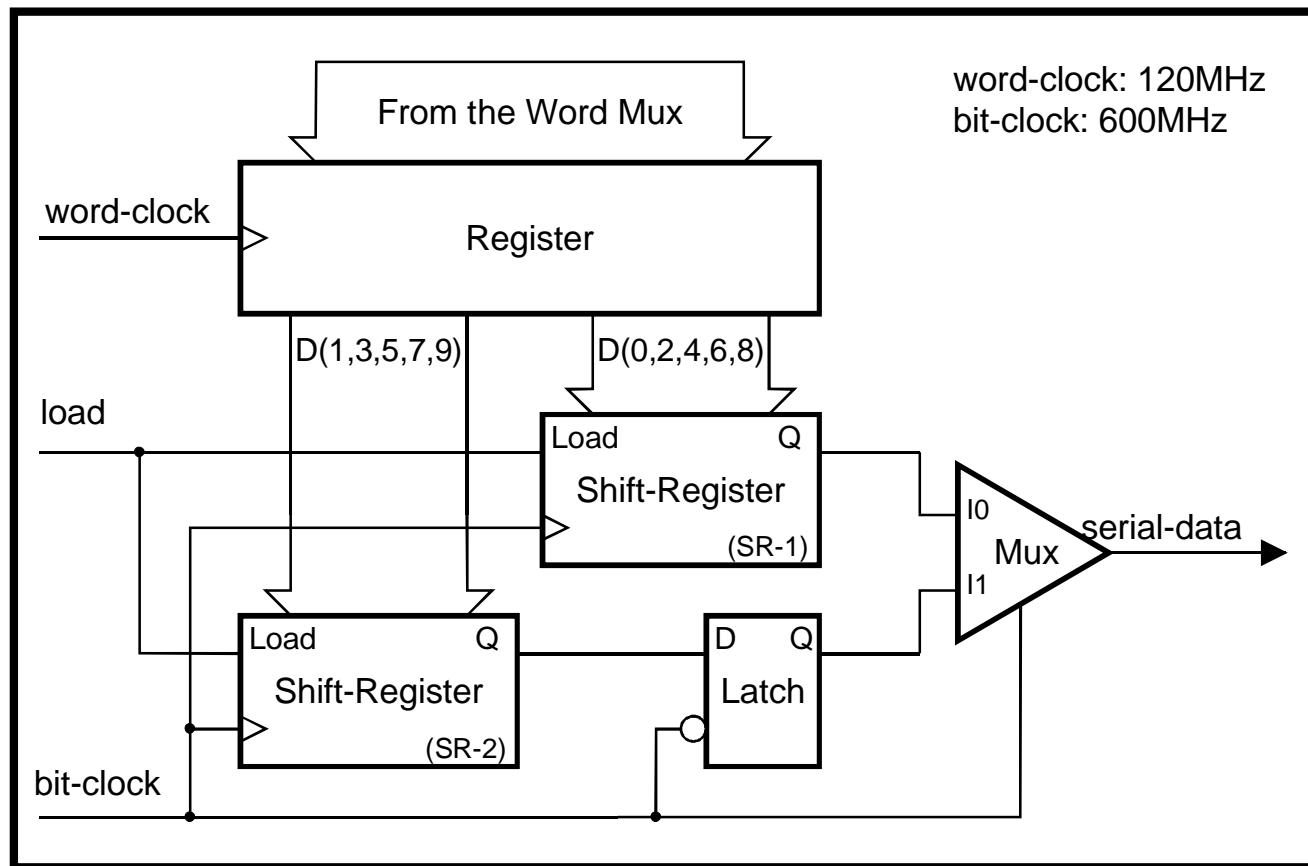

# ASIC Architecture

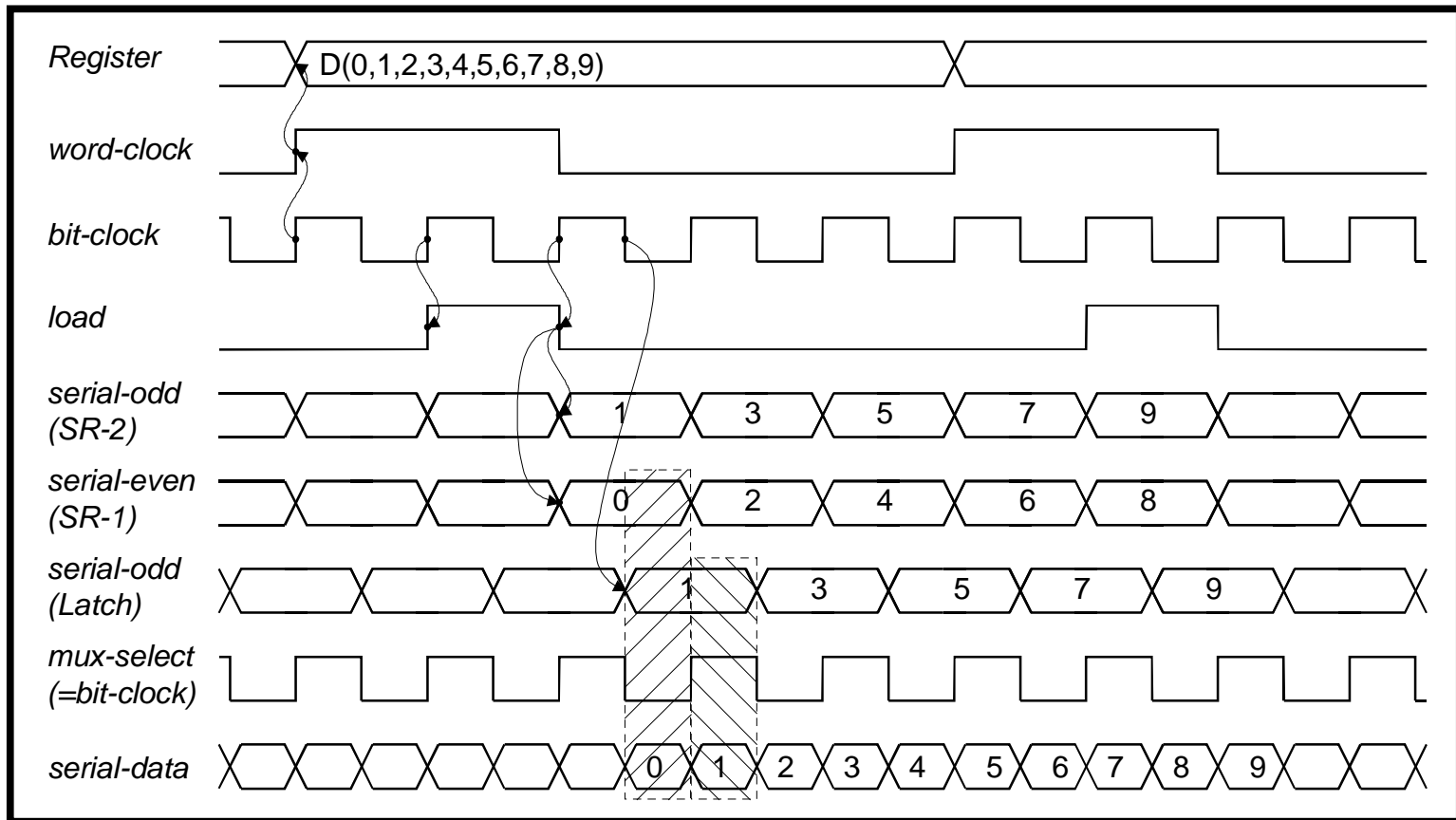

# ASIC Architecture

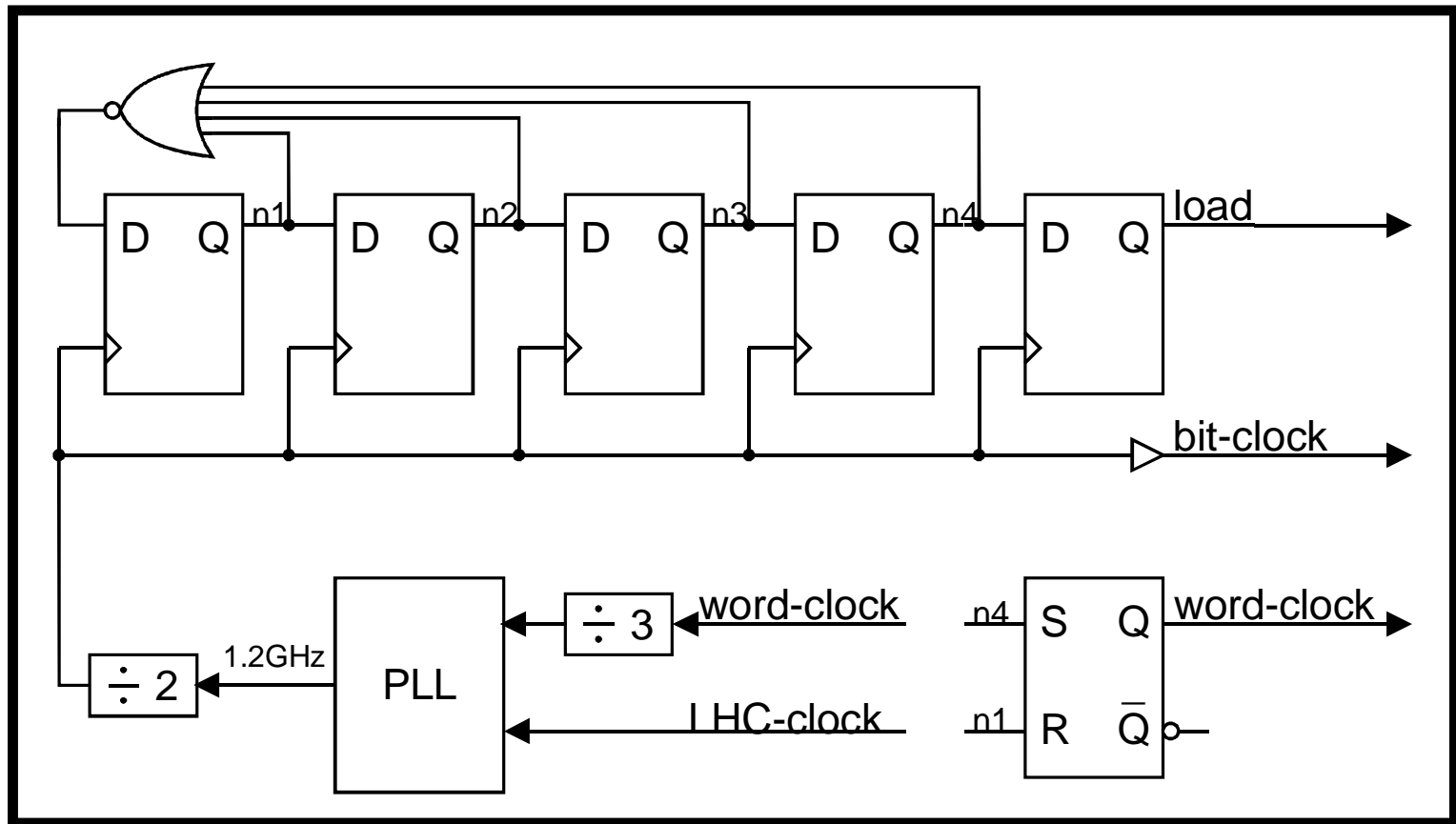


# ASIC Architecture

---


- The PLL
  - Classical structure
  - Three-state phase-frequency detector
  - Charge-pump
  - RC loop filter
  - Three differential cells with symmetrical loads

# ASIC Architecture

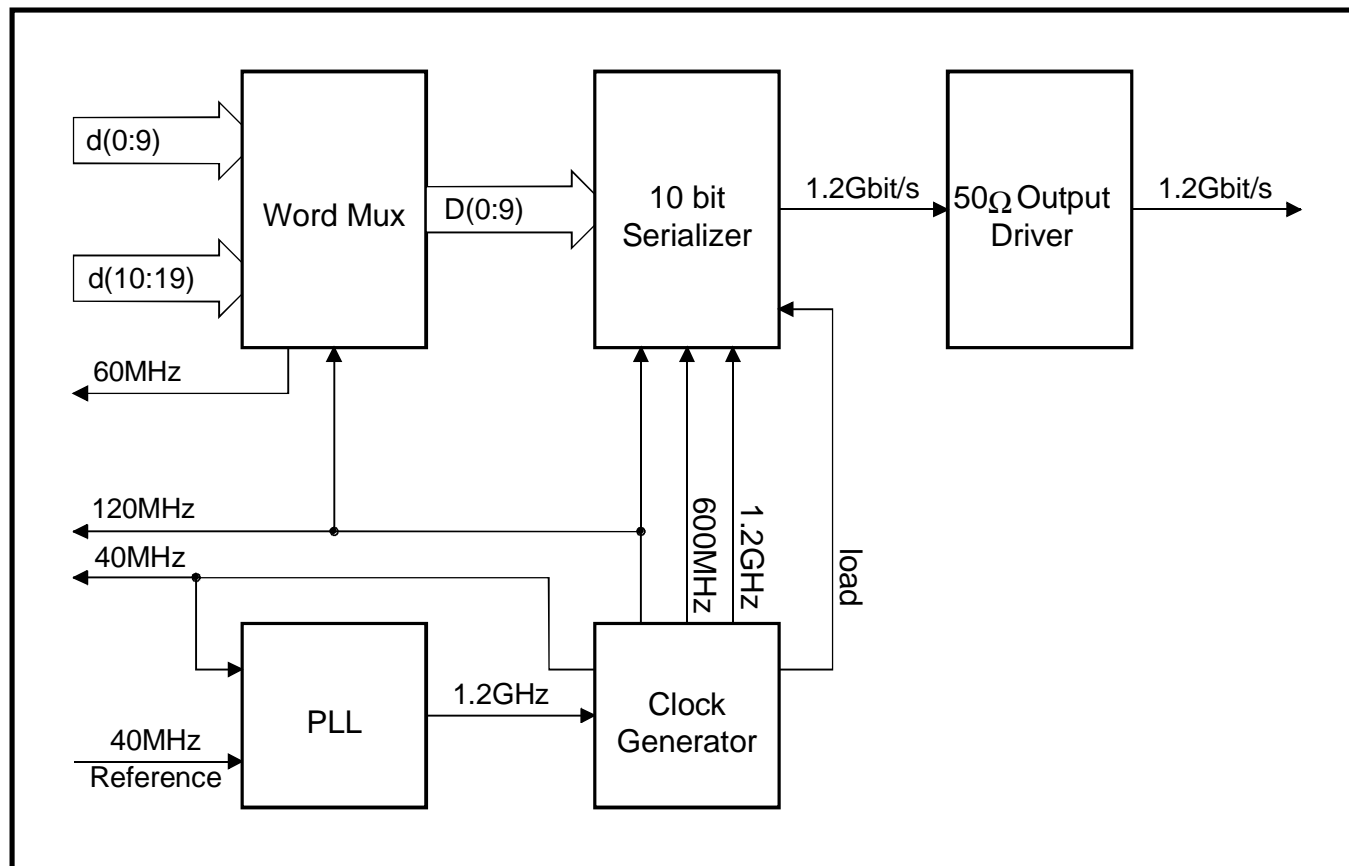



# Testing the IC

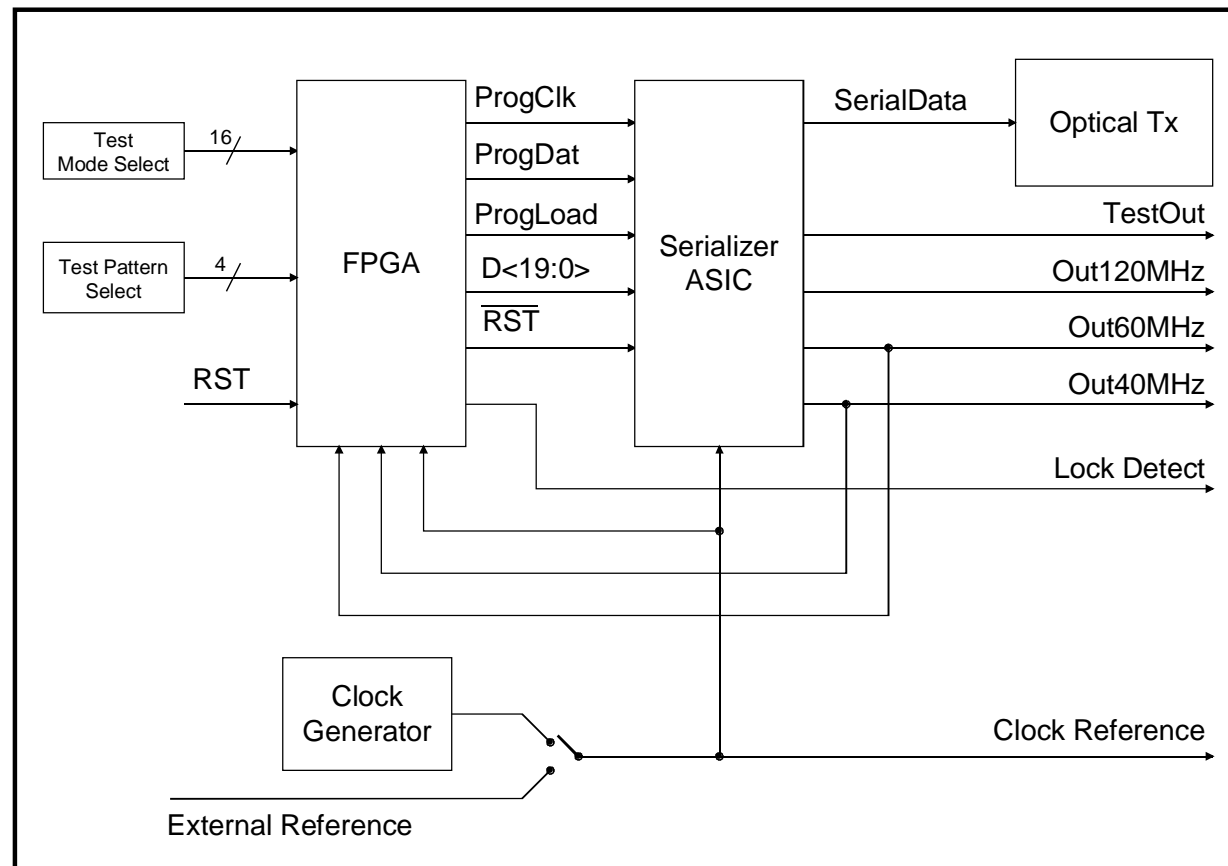

# Summary

---

- A 1.2GHz Serializer IC has been fabricated in 0.25 $\mu$ m CMOS
- The design uses radiation tolerant layout techniques
- A test setup has been developed using standard industrial components
- ...